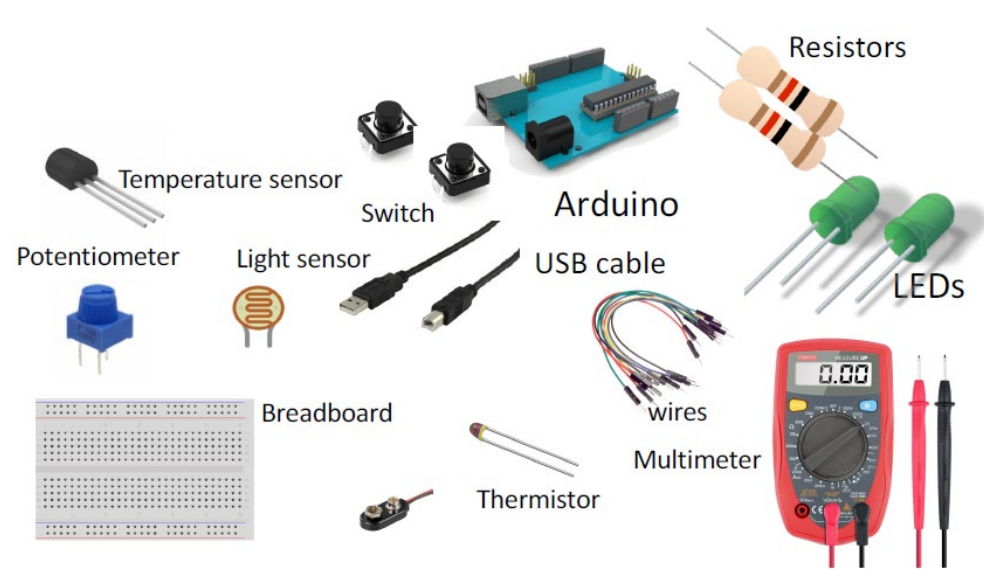


Smart Farm Basic Electronic

Dr. Jirapipat Thanyaphongphat







EQUIPMENT

Electrical Circuit



Here you see a basic Electrical Circuit:

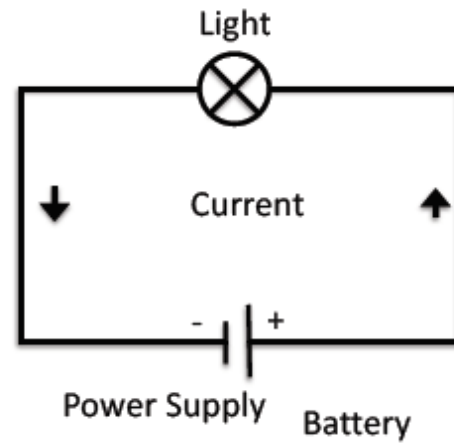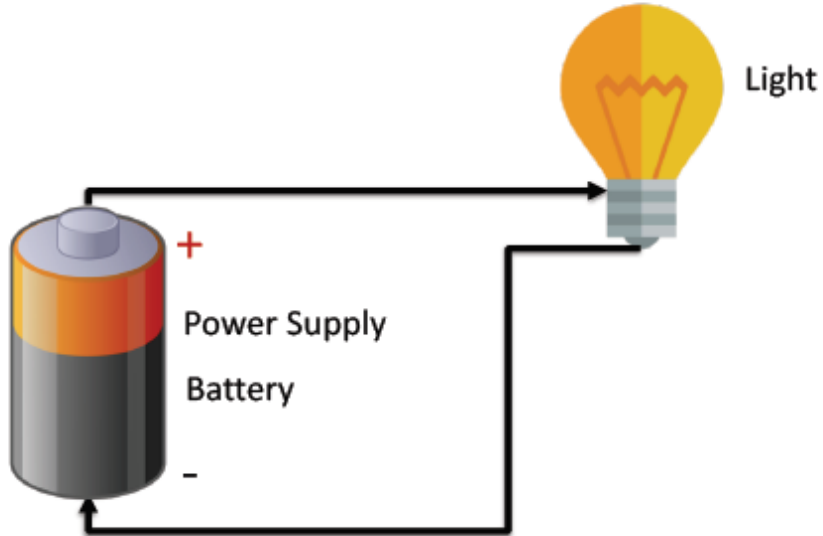

**ELECTRONICS
FOUNDATION**

Electrical Circuit with a Switch

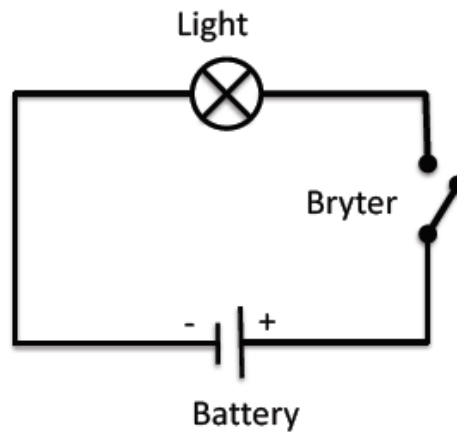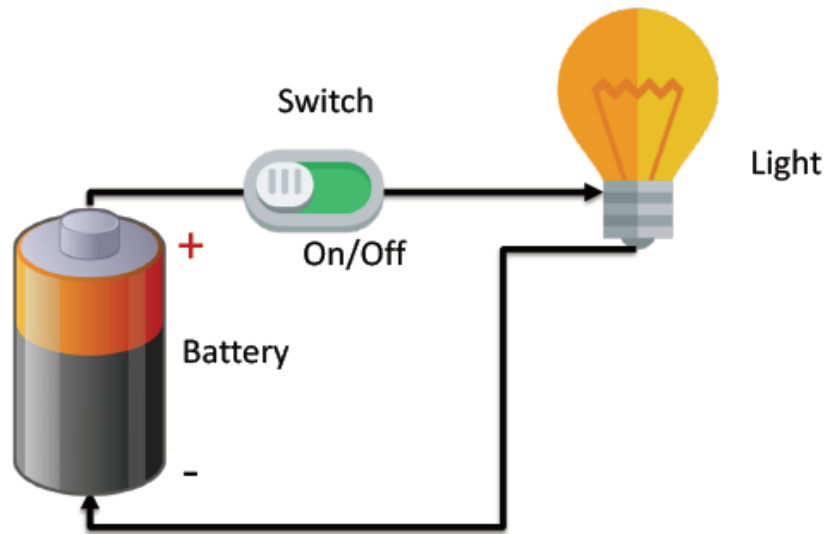Here you see a basic Electrical Circuit with a Switch:




**ELECTRONICS
FOUNDATION**

Short Circuit




- We must never connect positive and negative side to a power source without having an electrical component in between.
- If you do, it is called a short circuit.
- For example, if you short circuit a battery, the battery will get very hot and the battery will run out very quickly.
- Some batteries may also start to burn.
- When it starts to smoke from electrical components, it happens because it has become too hot.
- In most cases, it means that the component is broken.

Short Circuit!!

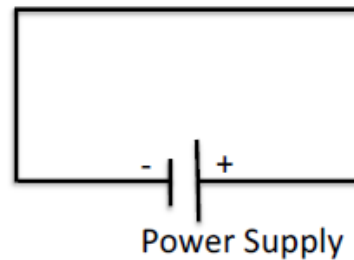

ELECTRONICS FOUNDATION

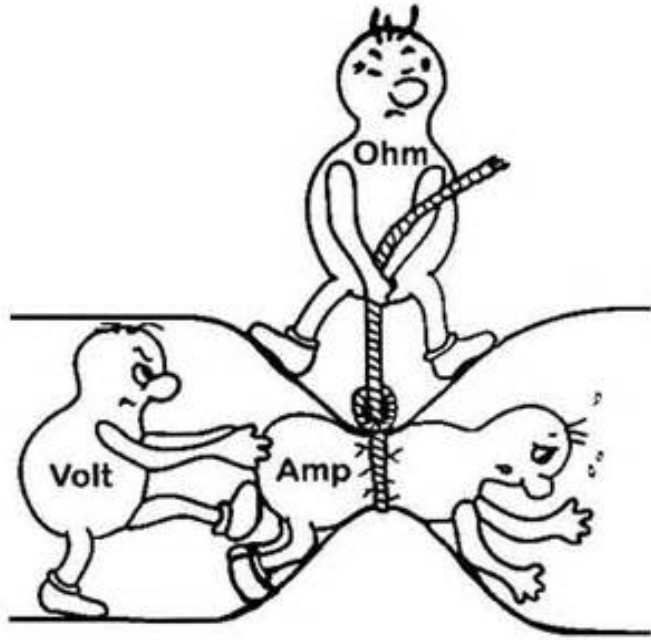


Ohms Law

This is Ohms Law:

$$U = RI$$

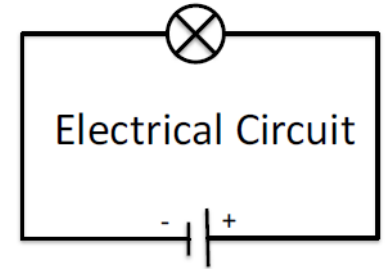U – Voltage [V]
 R – Resistance [Ω]
 I – Current [A]



$$R = \frac{U}{I}$$

$$I = \frac{U}{R}$$

ELECTRONICS FOUNDATION


Multimeter

You can use a Multimeter to measure current, voltage, resistance, etc. in an electric circuit.



**ELECTRONICS
FOUNDATION**

Light-Emitting Diode - LED

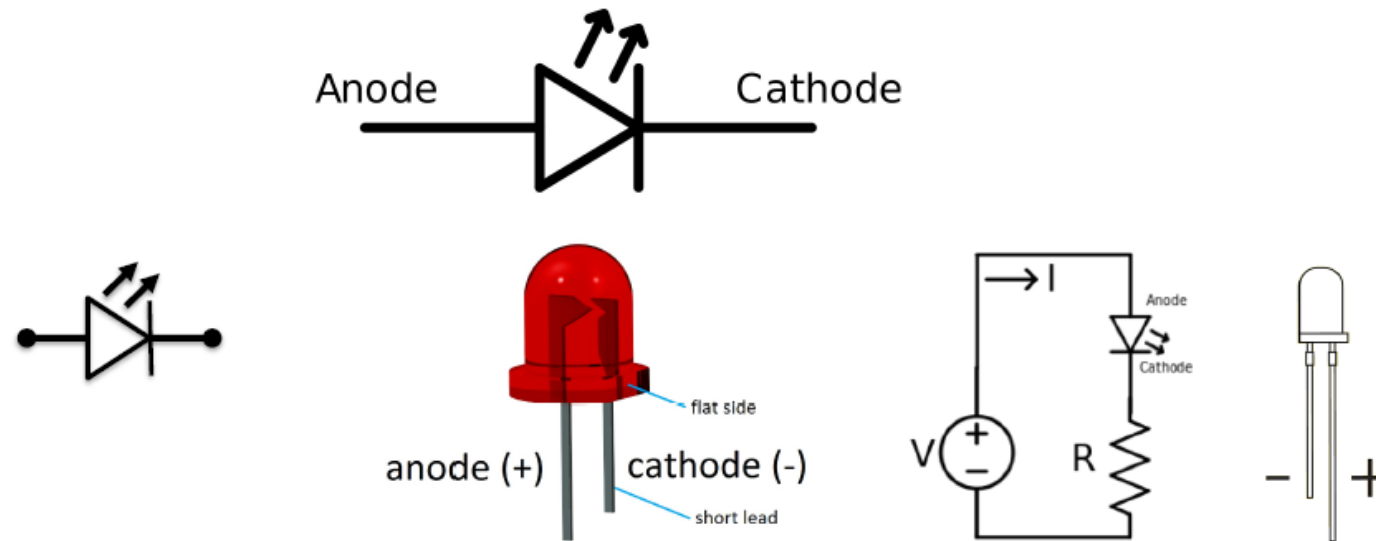

**ELECTRONICS
FOUNDATION**


Resistors

Resistance is measured in Ohm (Ω)

Resistors comes in many sizes, e.g., 220Ω , 270Ω , 330Ω , $1k\Omega$ $10k\Omega$, ...

The resistance can be found using Ohms Law

$$U = RI$$

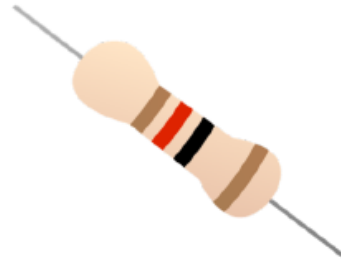



<https://en.wikipedia.org/wiki/Resistor>

Electrical symbol:



ELECTRONICS FOUNDATION

Resistor Color Codes

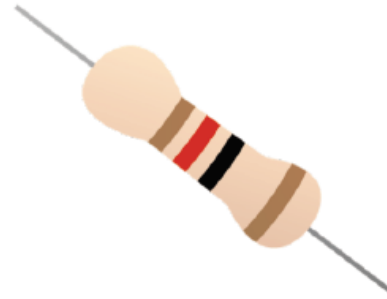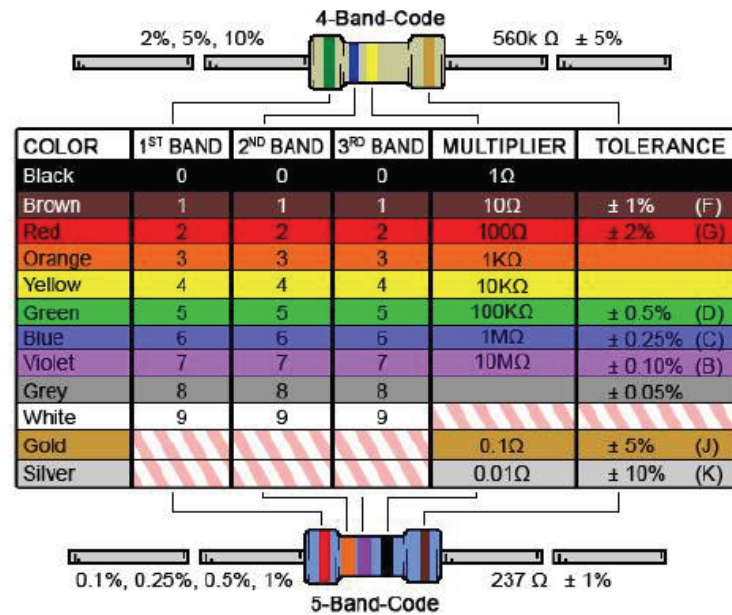

ELECTRONICS
FOUNDATION

Resistor Color Codes

TRY IT OUT!

What is the values for your resistors?

Use a «Resistor Color Code Calculator», which you can find on Internet




**ELECTRONICS
FOUNDATION**

Switch

A switch breaks the flow of current through a circuit when open. When closed, the current will flow unobstructed through the circuit.




A switch comes in many flavors

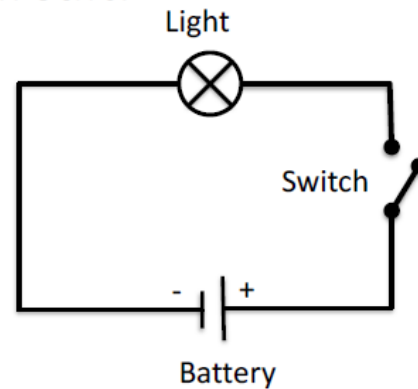


**ELECTRONICS
FOUNDATION**

Breadboard

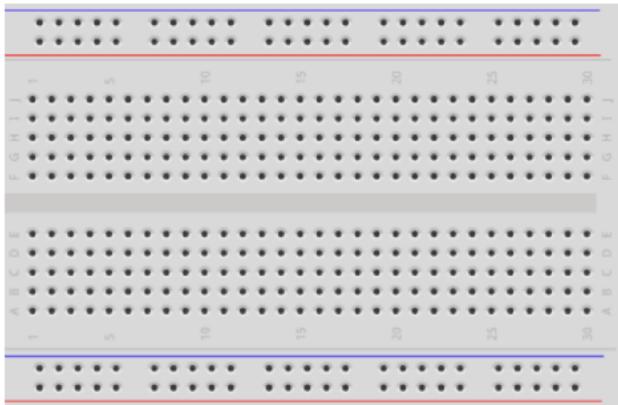




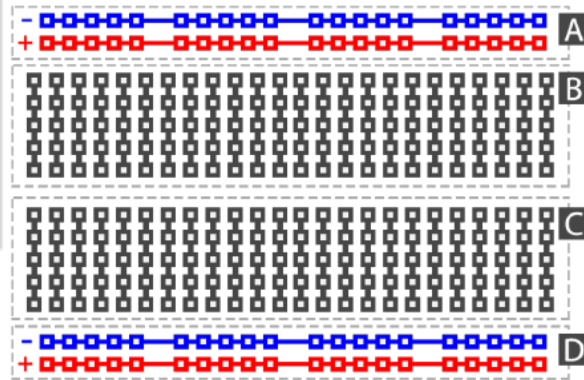
A breadboard is used to wire electric components together



**ELECTRONICS
FOUNDATION**

Breadboard – Correct Wiring

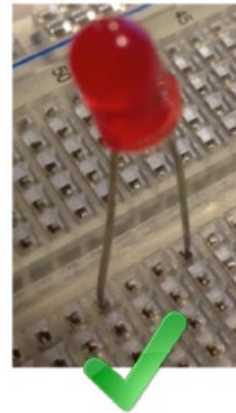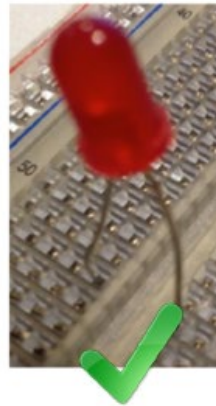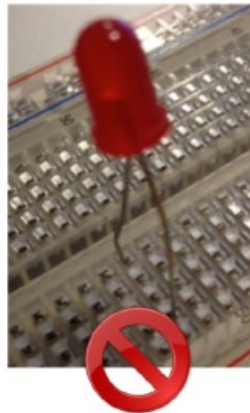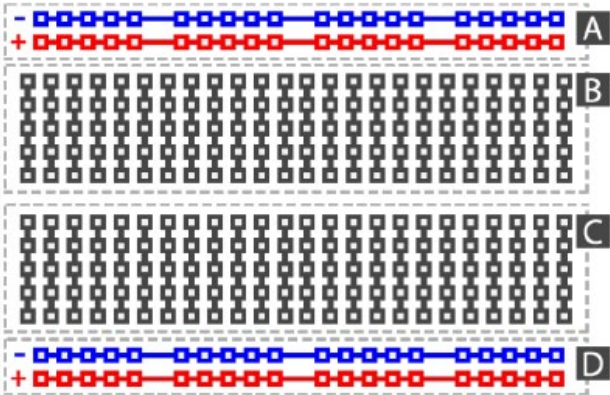Make sure not to short-circuit the components that you wire on the breadboard




ELECTRONICS FOUNDATION

PLAY AND EXPLORE

WWW.TINKERCAD.COM

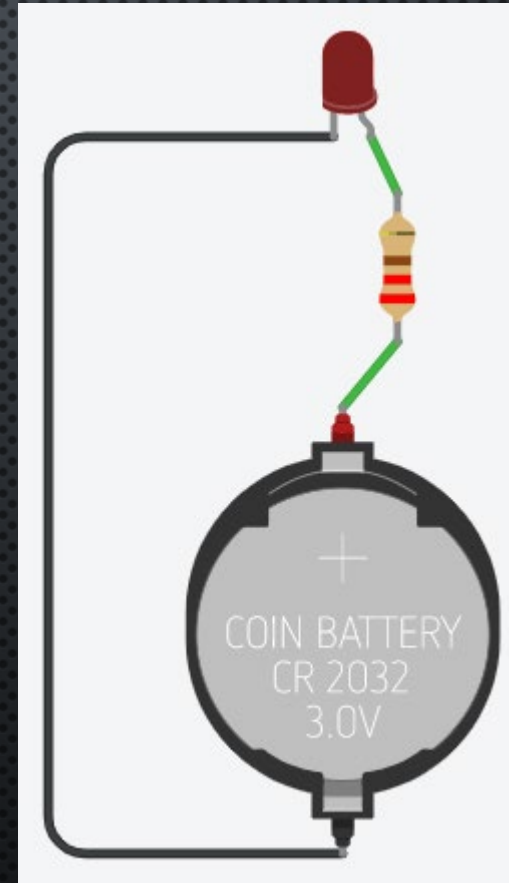
- Use the simulator to test your circuit design at any time.
- If you want to simulate other pre-made designs, check out the Starter Circuits, which you can find by clicking the "+ Components" button and then selecting the "Starter" tab.



PLAY AND EXPLORE



WWW.TINKERCAD.COM

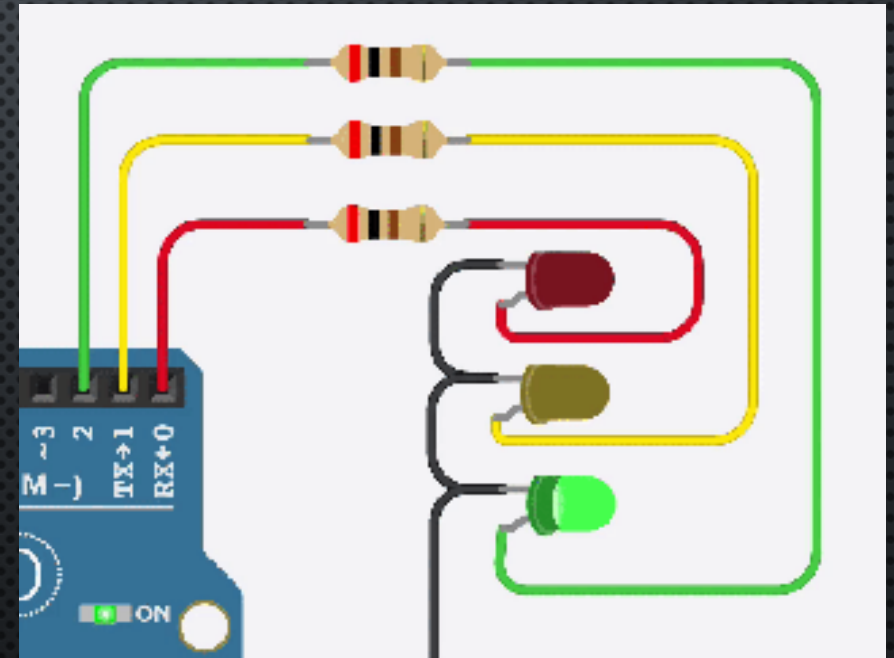- Use the simulator to test your circuit design at any time.
- If you want to simulate other pre-made designs, check out the Starter Circuits, which you can find by clicking the "+ Components" button and then selecting the "Starter" tab.





PLAY AND EXPLORE

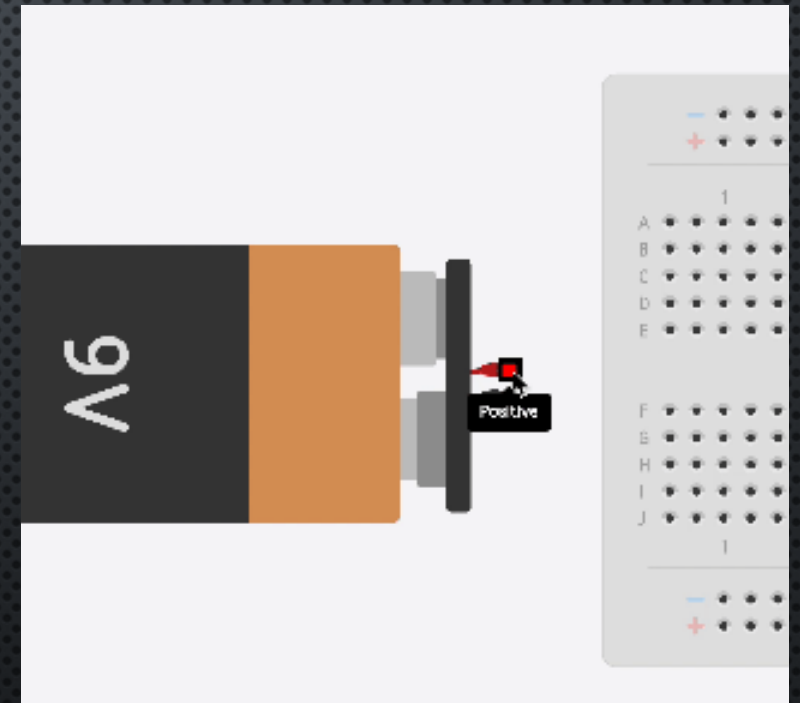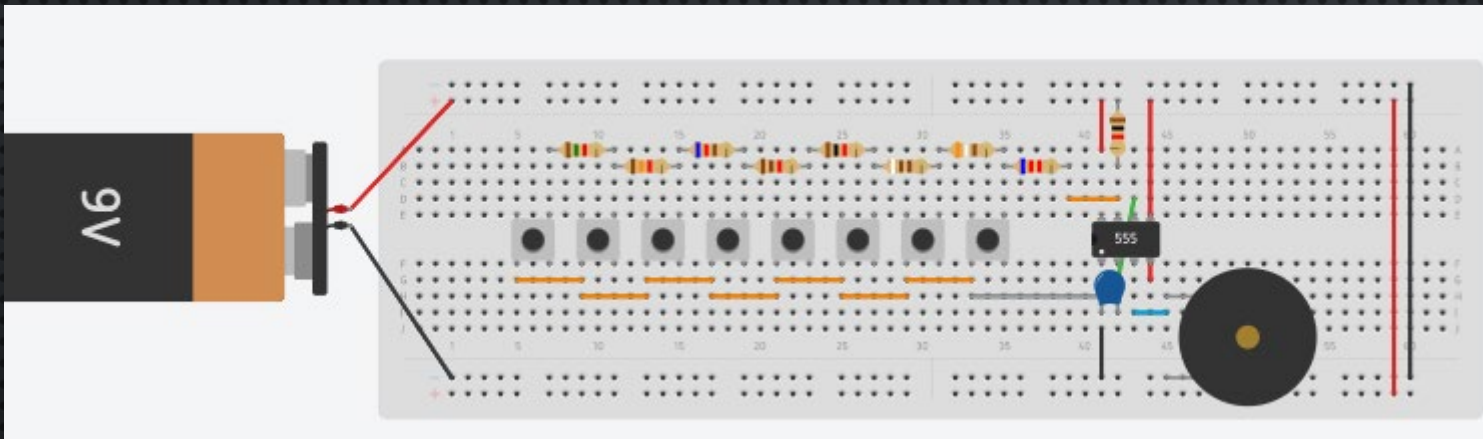- Wire the Positive and Negative Side of the Battery



PLAY AND EXPLORE

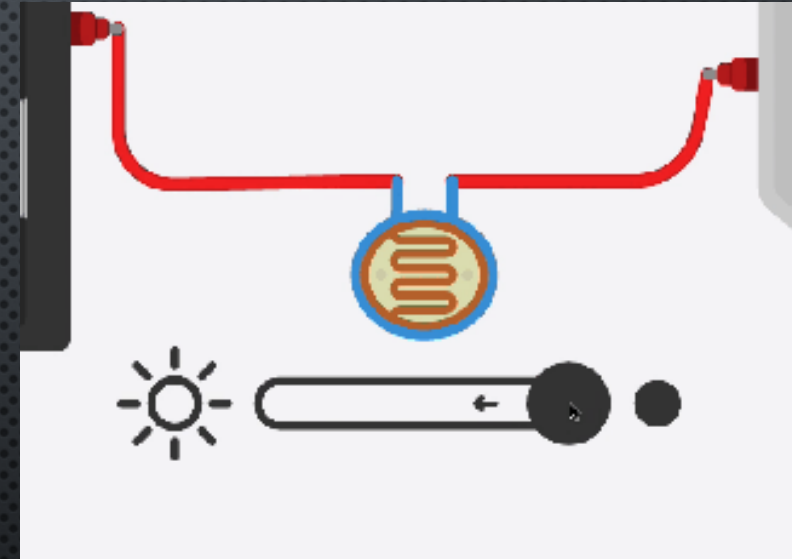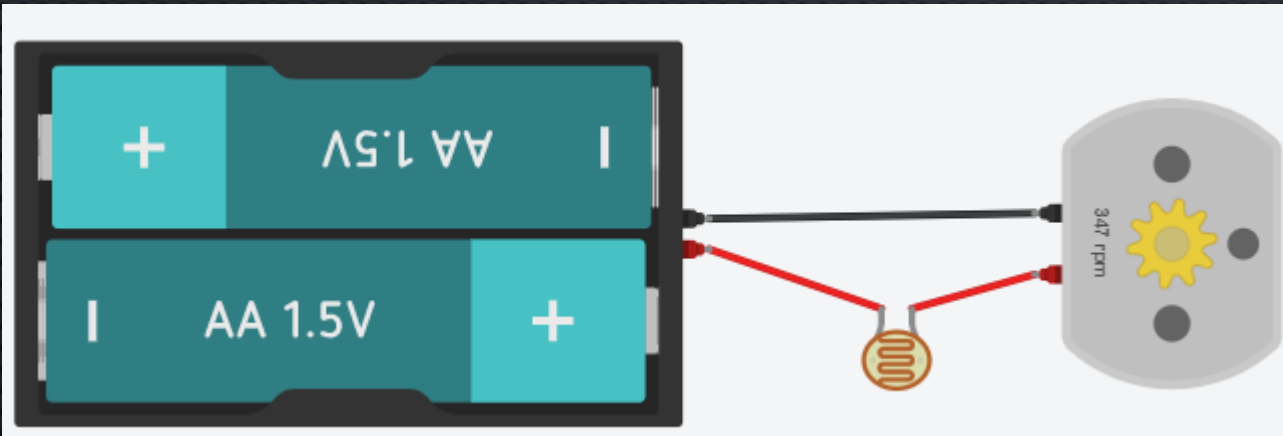
- How to add components to make an interactive motor controller.
- Add a Photoresistor



Electrical Cuircuit

TRY IT OUT!

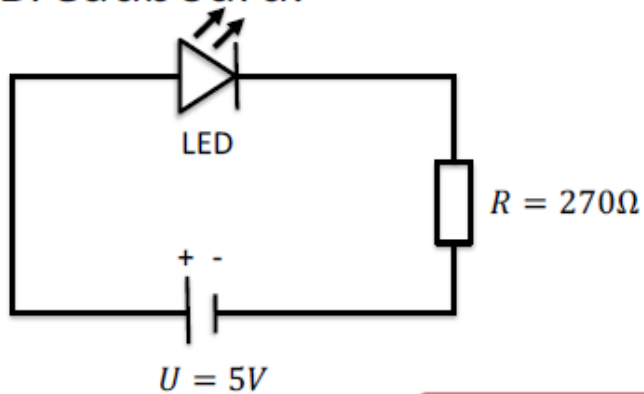Make the following circuit using the Arduino board and a Breadboard:



Equipment:

- Breadboard
- LED
- Resistor
- Wires
- Multi-meter

Example 1

Note! No Arduino Program is needed in this example

**FIND THE
RESISTOR
SIZE**

Why do you need a Resistor?



If the current becomes too large, the LED will be destroyed. To prevent this from happening, we will use a Resistor to limit the amount of current in the circuit.

What should be the size of the Resistor?

A LED typically needs a current like 20mA (can be found in the LED Datasheet).

We use Ohm's Law:

$$U = RI$$



Arduino gives $U=5V$ and $I=20mA$. We then get:

$$R = \frac{U}{I}$$



The Resistor needed will be $R = \frac{5V}{0.02A} = 250\Omega$. Resistors with $R=250\Omega$ are not so common, so we can use the closest Resistors we have, e.g., 270Ω

Example 1



FIND THE RESISTOR SIZE

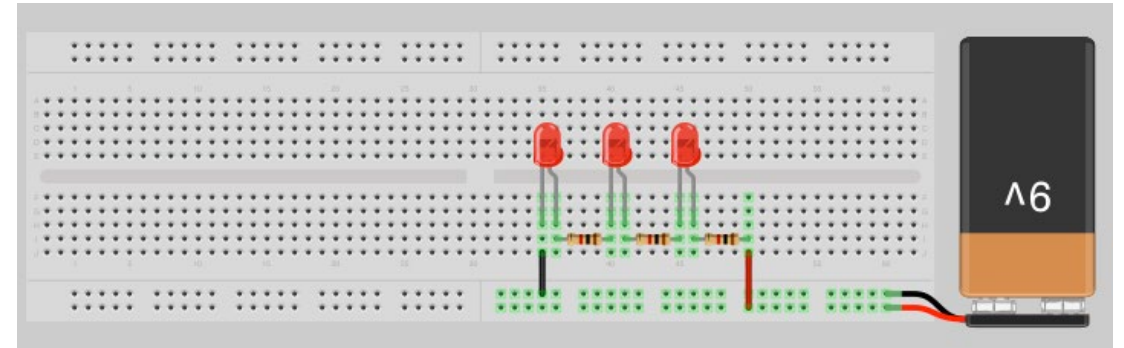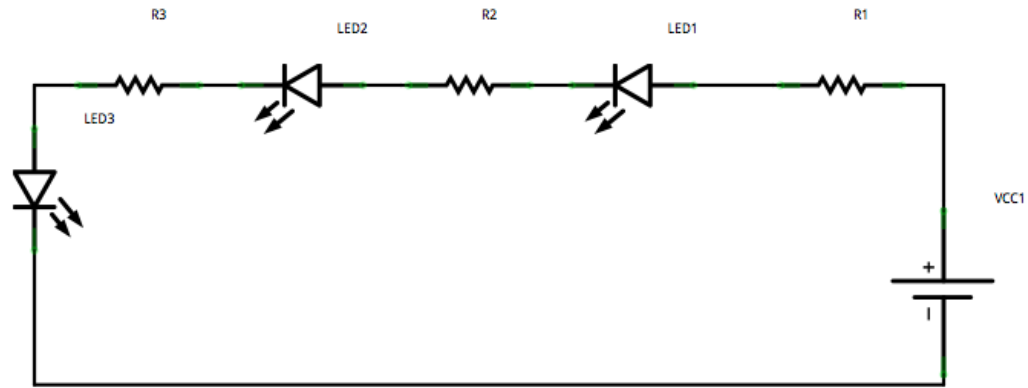

SERIES CIRCUIT EXAMPLE

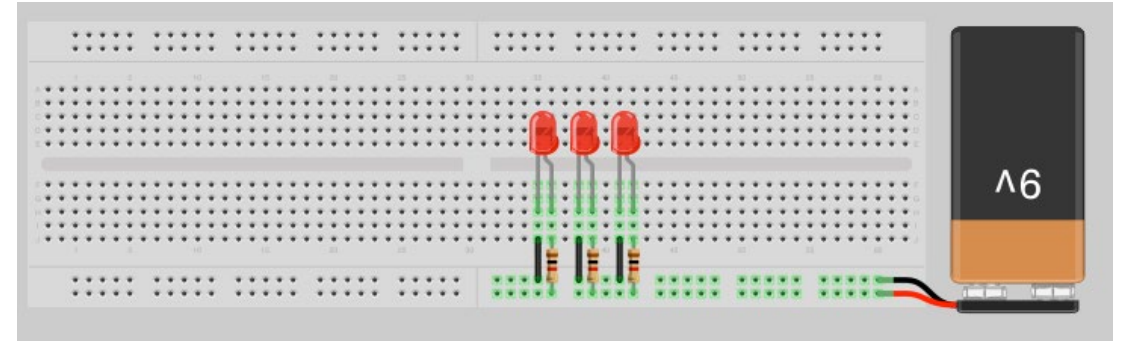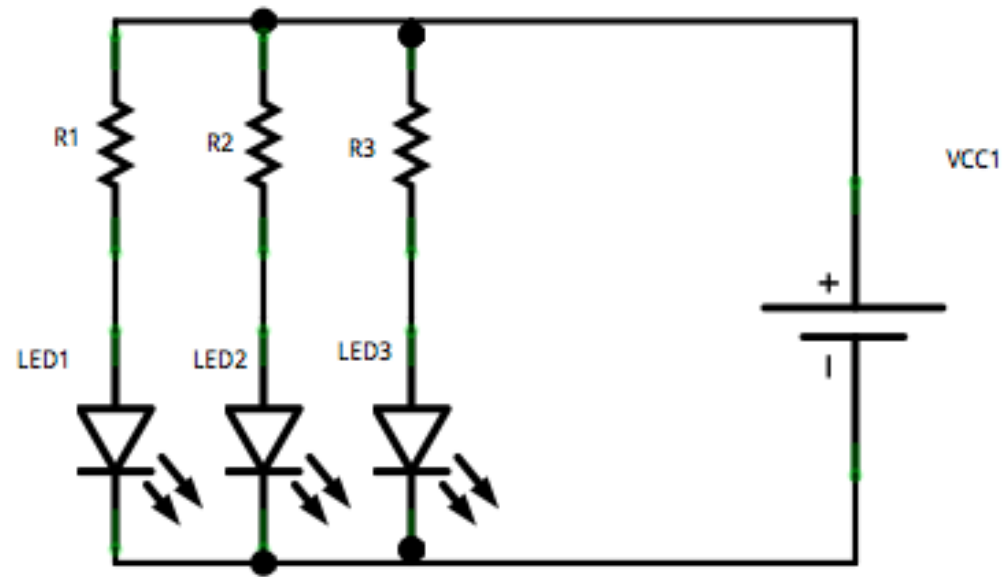

PARALLEL CIRCUIT EXAMPLE

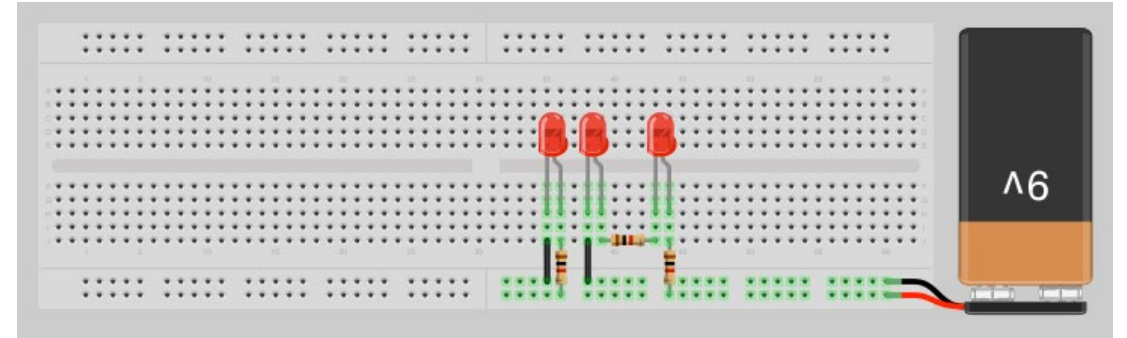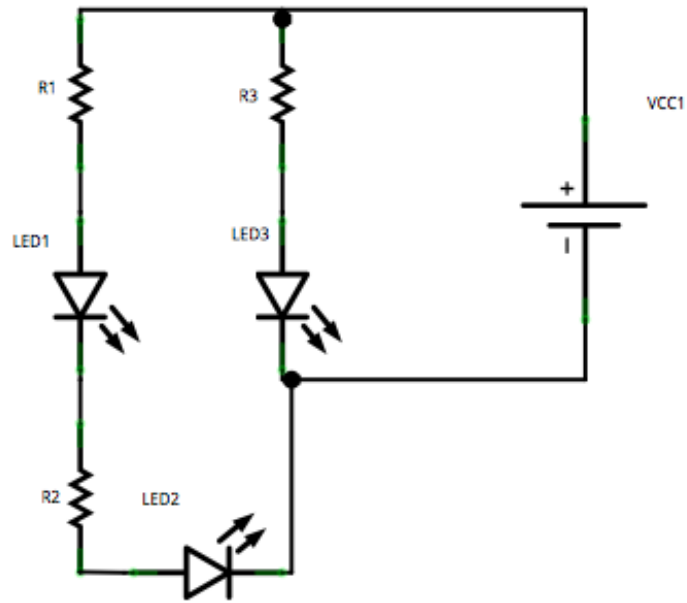

PARALLEL AND SERIES CIRCUIT EXAMPLE

ESP32 CPU

Arduino	ESP8266	ESP32
AVR ATMega328P	Tensilica Xtensa LX106	Tensilica Xtensa LX6
8 bit	32 bit	32 bit
1 core	1 core	2 core *
20 MHz	80/160 MHz	160/240 MHz
2 KB RAM	160 KB RAM	520 KB RAM
32 KB Flash	1 - 4 MB Flash	4 - 16 MB Flash

**ARDUINO-
ESP8266-
ESP32**



Q & A